

Signals and Communication II.

Dr. Ciira Maina
ciira.maina@dkut.ac.ke


12th January, 2021

Functions of a communication receiver

- ▶ Carrier frequency tuning
- ▶ Filtering
- ▶ Amplification


The superheterodyne receiver (superhet)

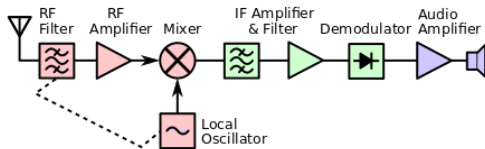- ▶ Achieves all three functions
- ▶ Overcomes difficulty of designing high-Q variable filters



Superheterodyne receiver - Source Wikipedia

Mixing

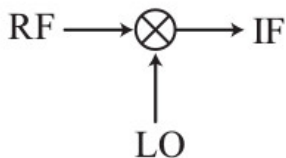

- ▶ An ideal mixer is represented by a multiplier symbol
- ▶ Let

$$v_{RF}(t) = A(t) \cos(2\pi f_{RF}t + \phi(t))$$
$$v_{LO} = A_{LO} \cos(2\pi f_{LO}t)$$

- ▶ The output of the mixer is given by

$$v_{out} = v_{RF}(t)v_{LO}(t)$$
$$=$$

Mixing


- ▶ The output of the mixer is given by

$$\begin{aligned}v_{out} &= v_{RF}(t)v_{LO}(t) \\ &= \frac{A(t)A_{LO}}{2} \left[\cos(2\pi(f_{RF} + f_{LO})t + \phi(t)) \right. \\ &\quad \left. + \cos(2\pi(f_{RF} - f_{LO})t + \phi(t)) \right]\end{aligned}$$

- ▶ The incoming RF has been translated into two frequencies $f_{RF} \pm f_{LO}$
- ▶ Here we assume $f_{LO} < f_{RF}$ which is known as lower side injection
- ▶ When $f_{LO} > f_{RF}$ it is known as upper side injection

Mixing

- ▶ Upper side injection.

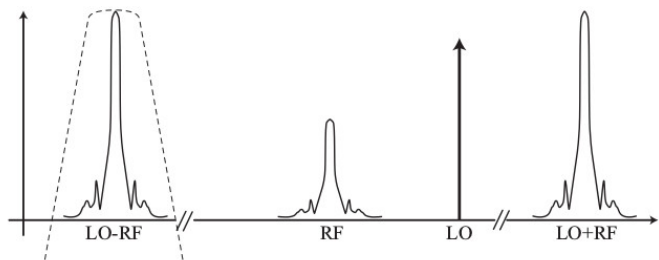

Intermediate Frequency

- ▶ The frequency $f_{RF} - f_{LO}$ or $f_{LO} - f_{RF}$ is known as the intermediate frequency.
- ▶ The IF section of the superhetro consists of a series of tuned amplifiers.

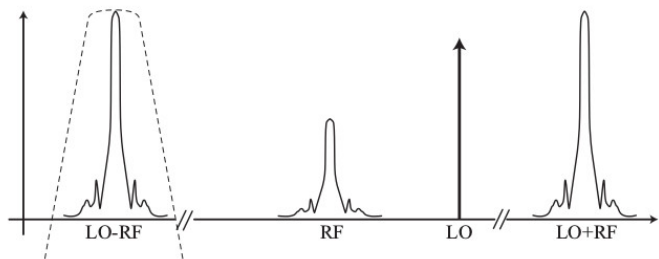


Image Frequency

- ▶ Radio frequencies given by $|f_{LO} \pm f_{IF}|$ result in signals at f_{IF} at the mixer output
- ▶ This is known as the image interference problem
- ▶ The RF section include an image rejection filter
- ▶ The bandwidth of this filter is approximately IF

Example

- ▶ Consider an FM signal at 101.1 MHz
- ▶ $f_{IF} = 10.7\text{MHz}$
- ▶ Assuming upper side injection, $f_{LO} = 111.8\text{MHz}$
- ▶ The image frequency is 122.5MHz

Example

- ▶ Consider an FM signal at 101.1 MHz
- ▶ $f_{IF} = 10.7\text{MHz}$
- ▶ Assuming lower side injection, $f_{LO} = ?$
- ▶ The image frequency is ?

Image Frequency Rejection

- ▶ To reject the image frequency a filter whose bandwidth is approximately IF is used in the RF section
- ▶ The Q of the filter is given by

$$Q = \frac{f_c}{BW}$$

- ▶ For FM systems, channel bandwidth is 200kHz, if we eliminate the IF section, we would need tunable filters with

$$Q \approx \frac{100 \times 10^6}{200 \times 10^3} = 500$$

- ▶ With an IF of 10MHz, the RF section filter Q is approximately 10
- ▶ High Q filters are expensive and difficult to design